

Elettronica dei Sistemi Digitali

Lab 03

Data-Path Elements



Gruppo: A11

Pronesti, Massimiliano	S245831
Oropallo, Maria Vittoria	S245999
Nicolicchia, Riccardo	S244728
Miceli, Michelangelo	S245478

8 aprile 2020

Indice

1	8-bit Sequential RCA	2
1.1	Spiegazione teorica	2
1.2	Procedimento	2
1.3	Risultati	4
1.4	Appendice	5
2	8-bit Sequential Adder/Subtractor	18
2.1	Spiegazione teorica	18
2.2	Procedimento	18
2.3	Risultati	19
2.4	Appendice	20
3	16-bit RCA, Carry-Bypass Adder and Carry-Select Adder	29
3.1	Spiegazione teorica	29
3.2	Procedimento	29
3.3	Risultati	30
3.4	Appendice	34
4	Multiplier	47
4.1	Spiegazione teorica	47
4.2	Procedimento	47
4.3	Risultati	49
4.4	Appendice	49

Capitolo 1

8-bit Sequential RCA

1.1 Spiegazione teorica

Ci si propone di realizzare un ripple-carry adder "sequenziale", ovvero un RCA i cui ingressi provengono da due registri di parallelismo 8 bit e le cui uscite vengono memorizzate su elementi di memoria.

1.2 Procedimento

Si costruisce un RCA mediante connessione di 8 full-adder, come mostrato in **figura 1.1**, optando per una implementazione tramite generics al fine di garantirne la riutilizzabilità nei successivi passi dell'esercitazione. Si è scelto, inoltre, di separare il componente dall'interfaccia tramite display, la cui tavola di verità è riportata in **figura 1.2**.

 


Figura 1.1: 8-bit full adder

$SW(3)$	$SW(2)$	$SW(1)$	$SW(0)$	a	b	c	d	e	f	g	HEX
0	0	0	0	0	0	0	0	0	0	1	0
0	0	0	1	1	0	0	1	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0	2
0	0	1	1	0	0	0	0	1	1	0	3
0	1	0	0	1	0	0	1	1	0	0	4
0	1	0	1	0	1	0	0	1	0	0	5
0	1	1	0	0	1	0	0	0	0	0	6
0	1	1	1	0	0	0	1	1	1	1	7
1	0	0	0	0	0	0	0	0	0	0	8
1	0	0	1	0	0	0	0	1	0	0	9
1	0	1	0	0	0	0	1	0	0	0	A
1	0	1	1	1	1	0	0	0	0	0	b
1	1	0	0	0	1	1	0	0	0	1	C
1	1	0	1	1	0	0	0	0	1	0	d
1	1	1	0	0	1	1	0	0	0	0	E
1	1	1	1	0	1	1	1	0	0	0	F

Figura 1.2: hex display truth table

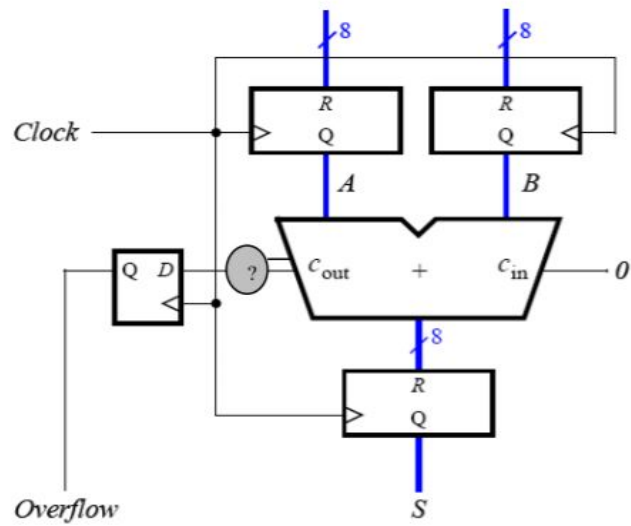


Figura 1.3: 8-bit registered-adder

1.3 Risultati

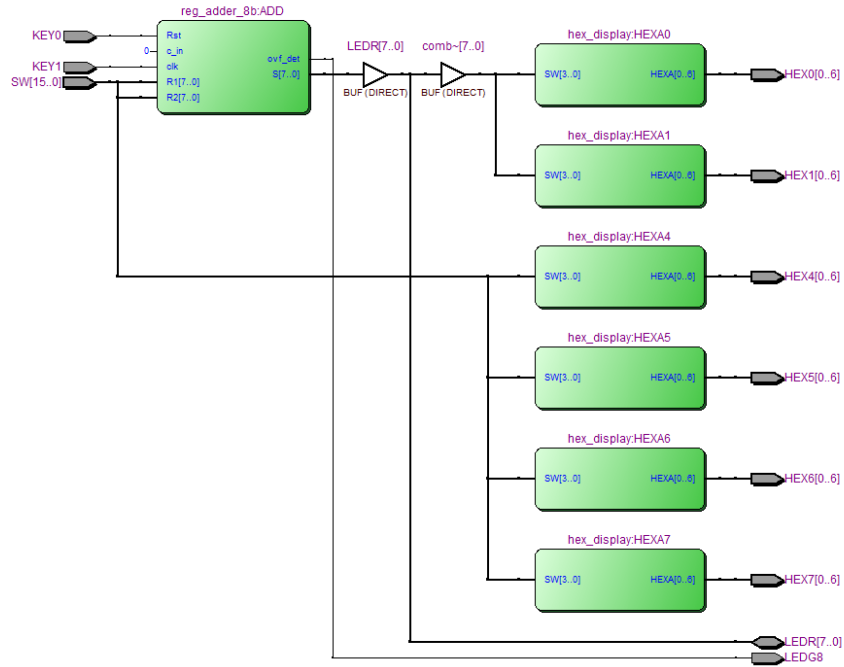


Figura 1.4: RTL viewer exercise no. 1


 


Figura 1.5: wave exercise no. 1

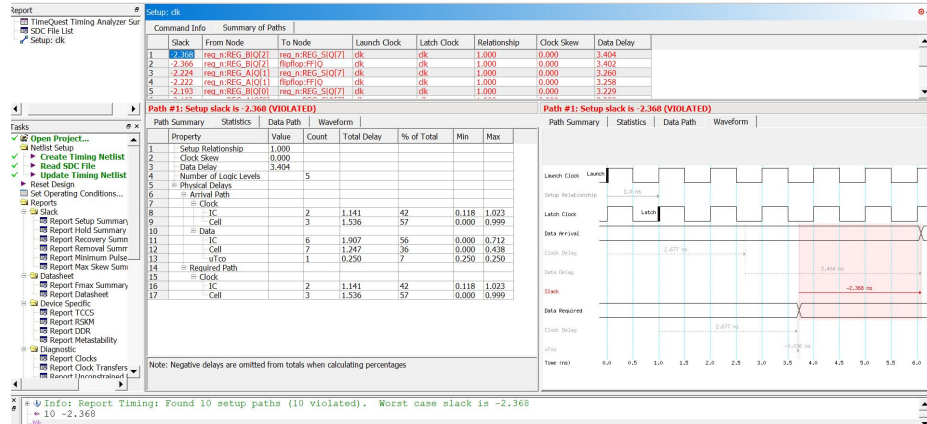Di seguito, infine, è riportata un'analisi temporale dell'andamento



laddove si evincono

$$f_{max} = 286.9 \text{ MHz}$$

$$t_{del} = 3.404 \text{ ns}$$

1.4 Appendice

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_adder_8b is
6
7     generic (n : integer := 8);
8
9     port ( R1,R2 : in signed ( n-1 downto 0 );
10           c_in : in std_logic;
11           clk,Rst : in std_logic;
12           c_out : out std_logic;
13           ovf_det : out std_logic;
14           S : out signed ( n-1 downto 0 )
15         );
16
17 end reg_adder_8b;
18
19 architecture struct of reg_adder_8b is
20
21     component flipflop
22         port (D, Clock, Resetn : in std_logic;
23              Q : out std_logic

```

```

24     );
25 end component;
26
27 component reg_n
28
29     generic ( N : integer:=n);
30
31     port (R : in signed(N-1 downto 0);
32           Clock, Resetn : in std_logic;
33           Q : out signed(N-1 downto 0)
34           );
35 end component;
36
37
38
39 component RCA
40
41     generic (n : integer := n);
42
43     port ( A,B : in signed ( n-1 downto 0 );
44           c_in : in std_logic;
45           c_out : out std_logic;
46           ovf_det : out std_logic;
47           S : out signed ( n-1 downto 0 )
48           );
49 end component;
50
51 signal A,B,Q : signed ( n-1 downto 0 );
52 signal ovf : std_logic;
53
54 begin
55
56     REG_A: reg_n port map ( R1,clk,Rst,A);
57     REG_B: reg_n port map ( R2,clk,Rst,B);
58
59     ADD: RCA port map ( A,B,c_in,c_out,ovf,Q );
60
61     FF: flipflop port map ( ovf,clk,Rst,ovf_det );
62
63     REG_S: reg_n port map (Q,clk,Rst,S);
64
65 end architecture;

```

Code 1.1: reg_adder_8b.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4

```

```

5  entity reg_adder_8b_tb is
6  end reg_adder_8b_tb;
7
8
9
10 architecture struct of reg_adder_8b_tb is
11
12     component reg_adder_8b
13         generic (n : integer := 8);
14
15         port ( R1,R2 : in signed ( n-1 downto 0 );
16               c_in : in std_logic;
17               clk,Rst : in std_logic;
18               c_out : out std_logic;
19               ovf_det : out std_logic;
20               S : out signed ( n-1 downto 0 )
21             );
22
23     end component;
24
25     signal A,B : signed ( 7 downto 0 );
26     signal A_int,B_int : integer;
27     signal c_out_dut,ovf_det_dut,clk,Rst : std_logic;
28     signal S_dut : signed ( 7 downto 0 );
29     signal S_int_dut,S_ref : integer;
30
31
32 begin
33
34     process begin
35         for i in 1 to 10 loop
36             clk <= '0';
37             wait for 2 ns;
38             clk <= '1';
39             wait for 2 ns;
40         end loop;
41     end process;
42
43     Rst <= '1','0' after 27 ns;
44
45     A <= "10111010", "01110110" after 5 ns, "01111101" after 9 ns,
46         "10101000" after 15 ns,
47         "11110111" after 21 ns, "01000111" after 25 ns;
48
49     B <= "00011010", "01100110" after 5 ns, "00011101" after 9 ns,
50         "11111000" after 15 ns,
51         "11110001" after 21 ns, "11010101" after 25 ns;
52
53     A_int <= to_integer(A);
54     B_int <= to_integer(B);

```



```

53
54
55     ADD: reg_adder_8b port map (A, B, '0', clk, Rst, c_out_dut,
        ovf_det_dut, S_dut);
56
57     S_int_dut <= to_integer(S_dut);
58     S_ref <= to_integer(A + B);
59
60 end architecture;

```

Code 1.2: reg_adder_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity adder_display is
6
7      --KEY -> clk, KEY0 -> RST, SW(15->8) -> A,
8      --SW(7->0) -> B, LEDR -> S, LEDG8 -> ovf_det,
9      --HEX7_6 -> A display, HEX5_4 -> B dspaly, HEX1_0 S_display
10     port (
11         SW : in signed ( 15 downto 0 );
12         KEY1,KEY0 : in std_logic;
13         LEDG8 : out std_logic;
14         LEDR : buffer signed ( 7 downto 0 );
15         HEX7,HEX6,HEX5,HEX4,HEX1,HEX0 : out std_logic_vector(0 to 6)
16     );
17 end adder_display;
18
19 architecture struct of adder_display is
20
21     component reg_adder_8b is
22         generic (n : integer := 8);
23
24         port ( R1,R2 : in signed ( n-1 downto 0 );
25             c_in : in std_logic;
26             clk,Rst : in std_logic;
27             c_out : out std_logic;
28             ovf_det : out std_logic;
29             S : out signed ( n-1 downto 0 )
30         );
31
32     end component;
33
34     component hex_display
35     port(
36         SW : in signed (3 downto 0);
37         HEXA : out std_logic_vector ( 0 to 6)

```

```

38     );
39     end component;
40
41
42 begin
43
44     ADD: reg_adder_8b port map(R1 => SW(15 downto 8), R2 => SW(7 downto 0),
45                               c_in => '0', clk => KEY1, Rst => KEY0,
46                               ovf_det => LEDG8, S => LEDR);
47
48     --A display
49     HEXA7: hex_display port map(SW(15 downto 12), HEX7);
50     HEXA6: hex_display port map(SW(11 downto 8), HEX6);
51
52     --B display
53     HEXA5: hex_display port map(SW(7 downto 4), HEX5);
54     HEXA4: hex_display port map(SW(3 downto 0), HEX4);
55
56     --S display
57     HEXA1: hex_display port map(LED7(7 downto 4), HEX1);
58     HEXA0: hex_display port map(LED7(3 downto 0), HEX0);
59
60
61 end architecture;

```

Code 1.3: adder_display.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity adder_display_tb is
6  end adder_display_tb;
7
8
9  architecture struct of adder_display_tb is
10
11     component adder_display
12     port (
13         SW : in signed ( 15 downto 0 );
14         KEY1, KEY0 : in std_logic;
15         LEDG8 : out std_logic;
16         LEDR : buffer signed ( 7 downto 0 );
17         HEX7, HEX6, HEX5, HEX4, HEX1, HEX0 : out std_logic_vector(0 to 6)
18     );
19     end component;
20
21     signal A : signed ( 7 downto 0 );
22     signal B : signed ( 7 downto 0 );

```

```

23  signal A_int,B_int : integer;
24  signal A_B : signed (15 downto 0);
25  signal ovf_det_dut,clk,Rst : std_logic;
26  signal S_dut : signed ( 7 downto 0 );
27  signal S_int_dut,S_ref : integer;
28  signal HEX7_dut,HEX6_dut,HEX5_dut,HEX4_dut,HEX1_dut,HEX0_dut :
      std_logic_vector(0 to 6);
29
30
31  begin
32
33      process begin
34          for i in 1 to 10 loop
35              clk <= '0';
36              wait for 2 ns;
37              clk <= '1';
38              wait for 2 ns;
39          end loop;
40      end process;
41
42      Rst <= '1','0' after 27 ns;
43
44      A <= "10111010", "01110110" after 5 ns, "01111101" after 9 ns,
          "10101000" after 15 ns,
45          "11110111" after 21 ns, "01000111" after 25 ns;
46
47      B <= "00011010", "01100110" after 5 ns, "00011101" after 9 ns,
          "11111000" after 15 ns,
48          "11110001" after 21 ns, "11010101" after 25 ns;
49
50      A_int <= to_integer(A);
51      B_int <= to_integer(B);
52      A_B <= A & B;
53
54      ADD: adder_display port map (A_B, clk, Rst, ovf_det_dut, S_dut,
55                                  HEX7_dut,HEX6_dut,HEX5_dut,HEX4_dut,HEX1_dut,HEX0_dut);
56
57      S_int_dut <= to_integer(S_dut);
58      S_ref <= to_integer(A + B) ;
59
60  end architecture;

```

Code 1.4: adder_display_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity RCA is

```

```

6  generic (n : integer := 8);
7  port ( A,B : in signed ( n-1 downto 0 );
8        c_in : in std_logic;
9        c_out : out std_logic;
10       ovf_det : out std_logic;
11       S : out signed ( n-1 downto 0 )
12     );
13
14  end RCA;
15
16  architecture struct of RCA is
17
18     component FA
19     port( a,b : in std_logic;
20          c_in : in std_logic;
21          s,c_out: out std_logic
22        );
23     end component;
24
25     signal carries : signed ( n downto 0);
26
27     begin
28     carries(0) <= c_in;
29
30     GEN : for i in 0 to n-1 generate
31         FULL_ADDERS: FA port map( A(i), B(i), carries(i), S(i),
32                                   carries(i+1));
33     end generate;
34
35     c_out <= carries(n);
36     ovf_det <= carries(n-1) xor carries(n);
37 end architecture;

```

Code 1.5: RCA.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity RCA_tb is
6  end RCA_tb;
7
8
9  architecture struct of RCA_tb is
10
11     component RCA
12     generic (n : integer := 8);
13
14     port ( A,B : in signed ( n-1 downto 0 );

```

```

15         c_in : in std_logic; --sub when add_sub == 1
16         c_out : out std_logic;
17         ovf_det : out std_logic;
18         S : out signed ( n-1 downto 0 )
19     );
20 end component;
21
22 signal A : signed ( 7 downto 0 );
23 signal B : signed ( 7 downto 0 );
24 signal A_int,B_int : integer;
25 signal c_out_dut,ovf_det_dut : std_logic;
26 signal S_dut : signed ( 7 downto 0 );
27 signal S_ref,S_int_dut : integer;
28
29
30 begin
31     process begin
32         -- generating signed numbers for testcases
33         for i in 2 to 4 loop
34
35             A <= to_signed(63*i, A'length);
36
37             for j in 0 to 2 loop
38                 B <= to_signed(61*j, B'length);
39                 wait for 5 ns;
40             end loop;
41
42         end loop;
43
44     end process;
45
46     A_int <= to_integer(A);
47     B_int <= to_integer(B);
48
49     ADD: RCA port map (A,B,'0',c_out_dut,ovf_det_dut,S_dut);
50
51     S_int_dut <= to_integer(S_dut);
52     S_ref <= to_integer(A + B) ;
53
54 end architecture;

```

Code 1.6: RCA_tb.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity FA is
5     port( a,b : in std_logic;
6           c_in : in std_logic;

```

```

7         s,c_out: out std_logic
8     );
9 end FA;
10
11
12 architecture struct of FA is
13
14     signal p : std_logic;
15
16     begin
17         p <= a xor b;
18         s <= c_in xor p;
19         c_out <= b when (p='0') else c_in;
20
21 end architecture;

```

Code 1.7: FA.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3
4
5 entity FA_tb is
6 end FA_tb;
7
8
9 architecture struct of FA_tb is
10
11     component FA
12     port( a,b : in std_logic;
13           c_in : in std_logic;
14           s,c_out: out std_logic
15         );
16     end component;
17
18     signal input_string : std_logic_vector(0 to 2);
19     signal s_dut,c_out_dut : std_logic;
20
21 begin
22
23     input_string <= "000","001" after 5 ns,"010" after 10 ns,
24                    "011" after 15 ns,"100" after 20 ns,
25                    "101" after 25 ns,"110" after 30 ns, "111" after 35 ns;
26
27     FULL_ADDER: FA port map(a => input_string(1),b => input_string(0),
28                             c_in => input_string(2),s => s_dut,c_out => c_out_dut);
29
30 end architecture;

```

Code 1.8: FA_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4
5  entity flipflop is
6      port (
7          D, Clock, Resetn : in std_logic;
8          Q : out std_logic
9      );
10 end flipflop;
11
12
13 architecture Behavior of flipflop is
14 begin
15
16     process (Clock, Resetn)
17     begin
18         if (Resetn = '0') then -- asynchronous clear
19             Q <= '0';
20         elsif (Clock'EVENT and Clock = '1') then
21             Q <= D;
22         end if;
23     end process;
24
25 end Behavior;

```

Code 1.9: flipflop.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5
6  entity reg_n is
7      generic ( N : integer:=8);
8      port (
9          R : in signed(N-1 downto 0);
10         Clock, Resetn : in std_logic;
11         Q : out signed(N-1 downto 0));
12 end reg_n;
13
14
15 architecture Behavior of reg_n is
16 begin
17
18     process (Clock, Resetn)
19     begin
20         if (Resetn = '0') then

```

```

21     Q <= (others => '0');
22     elsif (Clock'EVENT AND Clock = '1') then
23         Q <= R;
24     end if;
25 end process;
26
27 end Behavior;

```

Code 1.10: reg_n.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5
6  entity reg_n_tb is
7  end reg_n_tb;
8
9
10 architecture Behavior of reg_n_tb is
11
12     component reg_n is
13         generic ( N : integer:=3);
14
15         port (R : in signed(N-1 downto 0);
16              Clock, Resetn : in std_logic;
17              Q : out signed(N-1 downto 0)
18              );
19
20     end component;
21
22     signal clk : std_logic;
23     signal Rst : std_logic;
24     signal input_string : signed(2 downto 0);
25     signal out_dut : signed(2 downto 0);
26
27
28 begin
29
30     process begin
31         for i in 1 to 10 loop
32             clk <= '0';
33             wait for 1 ns;
34             clk <= '1';
35             wait for 1 ns;
36         end loop;
37     end process;
38
39     Rst <= '1','0' after 13 ns;

```



```

40
41     input_string <= "000", "001" after 4 ns,"010" after 8 ns,
42                     "011" after 9 ns, "100" after 11 ns;
43
44     REGN: reg_n port map(input_string,clk,Rst,out_dut);
45
46 end Behavior;

```

Code 1.11: reg_n.tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity hex_display is
6
7      port( SW : in signed (3 downto 0);
8            HEXA : out std_logic_vector ( 0 to 6)
9            );
10
11 end hex_display;
12
13
14 architecture behaviour of hex_display is
15
16 begin
17
18     with SW select
19         HEXA <=
20             "0000001" when "0000",
21             "1001111" when "0001",
22             "0010010" when "0010",
23             "0000110" when "0011",
24             "1001100" when "0100",
25             "0100100" when "0101",
26             "0100000" when "0110",
27             "0001111" when "0111",
28             "0000000" when "1000",
29             "0000100" when "1001",
30             "0001000" when "1010", -- A
31             "1100000" when "1011", -- b
32             "0110001" when "1100", -- C
33             "1000010" when "1101", -- d
34             "0110000" when "1110", -- E
35             "0111000" when "1111", -- F
36             "1111111" when others; --black for undefined values
37
38 end architecture;

```

Code 1.12: hex_display.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity hex_display_tb is
6  end hex_display_tb;
7
8
9  architecture behaviour of hex_display_tb is
10
11     component hex_display
12     port(
13         SW : in signed (3 downto 0);
14         HEXA : out std_logic_vector ( 0 to 6)
15     );
16     end component;
17
18     signal n_in : signed (3 downto 0);
19     signal out_dut : std_logic_vector (0 to 6);
20
21 begin
22     n_in <= "0000", "0001" after 5 ns, "0010" after 10 ns, "0011" after 15
        ns,
23         "0100" after 20 ns, "0101" after 25 ns, "0110" after
        30 ns,
24         "0111" after 35 ns, "1000" after 40 ns, "1001" after
        45 ns,
25         "1010" after 50 ns, "1011" after 55 ns, "1100" after
        60 ns,
26         "1101" after 65 ns, "1110" after 70 ns, "1111" after
        75 ns;
27
28     DISPLAY: hex_display port map (n_in,out_dut);
29
30 end architecture;

```

Code 1.13: hex_display_tb.vhd

Capitolo 2

8-bit Sequential Adder/Subtractor

2.1 Spiegazione teorica

Si modifica il precedente RCA in modo che esso permetta di svolgere anche la sottrazione.

2.2 Procedimento

 


Figura 2.1: 2's n-bit adder/subtractor

Si realizza lo schema a blocchi mostrato in **figura 2.1**. L'aggiunta delle porte XOR, se il segnale di SUB è attivo, complementa il secondo ingresso (vettoriale) eseguendo così una sottrazione. Viceversa, i due ingressi sono addizionati.

2.3 Risultati

 


Figura 2.2: wave exercise no. 2


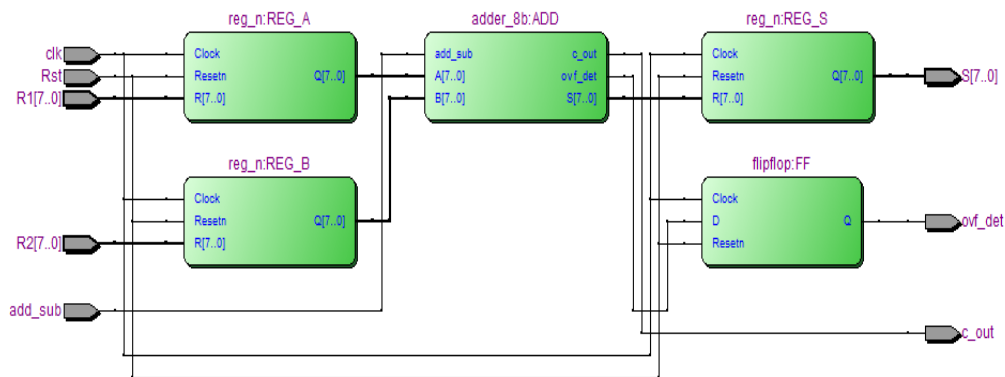


Figura 2.3: RTL viewer exercise no. 2

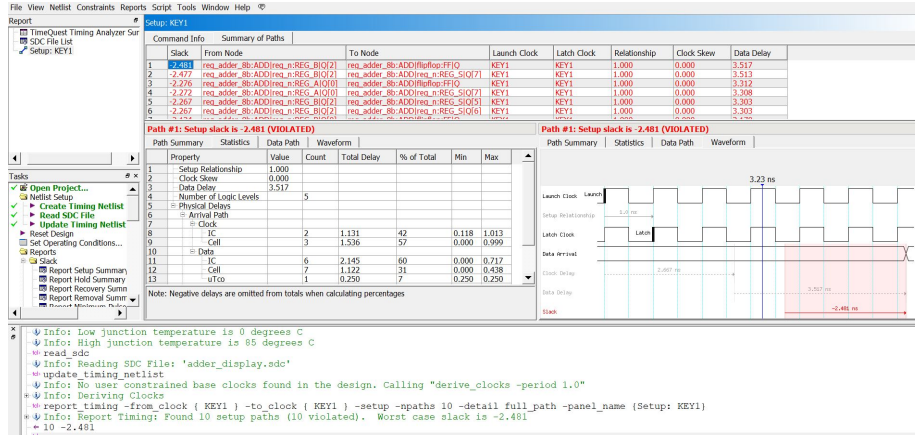Di seguito, infine, è riportata l'analisi temporale



laddove si evince

$$f_{max} = 287.3 \text{ MHz}$$

$$t_{del} = 3.517 \text{ ns}$$

2.4 Appendice

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_adder_8b is
6     generic (n : integer := 8);
7
8     port ( R1,R2 : in signed ( n-1 downto 0 );
9           add_sub : in std_logic;
10          clk,Rst : in std_logic;
11          c_out : out std_logic;
12          ovf_det : out std_logic;
13          S : out signed ( n-1 downto 0 )
14        );
15 end reg_adder_8b;
16
17
18 architecture struct of reg_adder_8b is
19
20     component flipflop
21         port (D, Clock, Resetn : in std_logic;
22              Q : out std_logic
23             );
24     end component;

```

```

25
26     component reg_n
27         generic ( N : integer:=n);
28
29         port (R : in signed(N-1 downto 0);
30              Clock, Resetn : in std_logic;
31              Q : out signed(N-1 downto 0)
32              );
33     end component;
34
35
36
37     component adder_8b
38         generic (n : integer := n);
39
40         port ( A,B : in signed ( n-1 downto 0 );
41              add_sub : in std_logic;
42              c_out : out std_logic;
43              ovf_det : out std_logic;
44              S : out signed ( n-1 downto 0 )
45              );
46     end component;
47
48     signal A,B,Q : signed ( n-1 downto 0 );
49     signal ovf : std_logic;
50
51 begin
52
53     REG_A: reg_n port map ( R1,clk,Rst,A);
54     REG_B: reg_n port map ( R2,clk,Rst,B);
55
56     ADD: adder_8b port map ( A,B,add_sub,c_out,ovf,Q );
57
58     FF: flipflop port map ( ovf,clk,Rst,ovf_det );
59
60     REG_S: reg_n port map (Q,clk,Rst,S);
61
62 end architecture;

```

Code 2.1: reg_adder_8b.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_adder_8b_tb is
6 end reg_adder_8b_tb;
7
8

```

```

9
10 architecture struct of reg_adder_8b_tb is
11
12     component reg_adder_8b
13         generic (n : integer := 8);
14
15         port ( R1,R2 : in signed ( n-1 downto 0 );
16               add_sub : in std_logic;
17               clk,Rst : in std_logic;
18               c_out : out std_logic;
19               ovf_det : out std_logic;
20               S : out signed ( n-1 downto 0 )
21             );
22     end component;
23
24     signal A,B : signed ( 7 downto 0 );
25     signal A_int,B_int : integer;
26     signal add_sub,c_out_dut,ovf_det_dut,clk,Rst : std_logic;
27     signal S_dut : signed ( 7 downto 0 );
28     signal S_int_dut,S_ref : integer;
29
30
31 begin
32
33     process begin
34         for i in 1 to 10 loop
35             clk <= '0';
36             wait for 2 ns;
37             clk <= '1';
38             wait for 2 ns;
39         end loop;
40     end process;
41
42     Rst <= '1','0' after 27 ns;
43
44     add_sub <= '0', '1' after 16 ns;
45
46     A <= "10111010", "01110110" after 5 ns, "01111101" after 9 ns,
47         "10101000" after 15 ns,
48         "11110111" after 21 ns, "01000111" after 25 ns;
49
50     B <= "00011010", "01100110" after 5 ns, "00011101" after 9 ns,
51         "11111000" after 15 ns,
52         "11110001" after 21 ns, "11010101" after 25 ns;
53
54     A_int <= to_integer(A);
55     B_int <= to_integer(B);
56
57     ADD: reg_adder_8b port map (A, B, add_sub, clk, Rst, c_out_dut,

```

```

        ovf_det_dut, S_dut);
57
58     S_int_dut <= to_integer(S_dut);
59
60     with add_sub select
61         S_ref <=
62             to_integer(A + B) when '0',
63             to_integer(A - B) when others;
64
65 end architecture;

```

Code 2.2: reg_adder_8b_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity adder_8b is
6      generic (n : integer := 8);
7
8      port ( A,B : in signed ( n-1 downto 0 );
9            add_sub : in std_logic; --sub when add_sub == 1
10           c_out : out std_logic;
11           ovf_det : out std_logic;
12           S : out signed ( n-1 downto 0 )
13       );
14
15 end adder_8b;
16
17 architecture struct of adder_8b is
18
19     component FA
20         port( a,b : in std_logic;
21              c_in : in std_logic;
22              s,c_out: out std_logic
23         );
24     end component;
25
26     signal carries : signed ( n downto 0);
27     signal b_pos_neg : signed ( n-1 downto 0);
28
29
30 begin
31     carries(0) <= add_sub;
32
33     GEN: for i in 0 to n-1 generate
34
35         b_pos_neg(i) <= add_sub xor B(i);
36         FULL_ADDERS: FA port map( A(i), b_pos_neg(i), carries(i), S(i),

```



```

        carries(i+1));
37
38     end generate;
39
40     c_out <= carries(n);
41     ovf_det <= carries(n-1) xor carries(n);
42
43 end architecture;

```

Code 2.3: adder_8b.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity adder_8b_tb is
6  end adder_8b_tb;
7
8
9  architecture struct of adder_8b_tb is
10
11     component adder_8b
12         generic (n : integer := 8);
13
14         port ( A,B : in signed ( n-1 downto 0 );
15               add_sub : in std_logic; --sub when add_sub == 1
16               c_out : out std_logic;
17               ovf_det : out std_logic;
18               S : out signed ( n-1 downto 0 )
19             );
20     end component;
21
22     signal A : signed ( 7 downto 0 );
23     signal B : signed ( 7 downto 0 );
24     signal A_int,B_int : integer;
25     signal add_sub : std_logic;
26     signal c_out_dut,ovf_det_dut : std_logic;
27     signal S_dut : signed ( 7 downto 0 );
28     signal S_ref,S_int_dut : integer;
29
30
31
32 begin
33
34     add_sub <= '0', '1' after 16 ns;
35
36     process begin
37         for i in 2 to 4 loop
38

```

```

39         A <= to_signed(63*i, A'length);
40
41         for j in 0 to 2 loop
42
43             B <= to_signed(61*j, B'length);
44             wait for 2 ns;
45
46         end loop;
47
48     end loop;
49
50 end process; A_int <= to_integer(A);
51 B_int <= to_integer(B);
52
53 ADD: adder_8b port map (A,B,add_sub,c_out_dut,ovf_det_dut,S_dut);
54
55 S_int_dut <= to_integer(S_dut);
56
57 with add_sub select
58     S_ref <=
59         to_integer(A + B) when '0',
60         to_integer(A - B) when others;
61
62 end architecture;

```

Code 2.4: adder_8b.tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity adder_display is
6
7      --KEY -> clk, KEY0 -> RST, SW(16) -> add_sub,SW(15->8) -> A,
8      --SW(7->0) ->B,LEDR ->S,LEDG8 -> ovf_det,
9      --HEX7_6 -> A display, HEX5_4 -> B dspaly, HEX1_0 S_display
10     port ( SW : in signed ( 16 downto 0 );
11           KEY1,KEY0 : in std_logic;
12           LEDG8 : out std_logic;
13           LEDR : buffer signed ( 7 downto 0 );
14           HEX7,HEX6,HEX5,HEX4,HEX1,HEX0 : out std_logic_vector(0 to 6)
15
16     );
17 end adder_display;
18
19 architecture struct of adder_display is
20
21     component reg_adder_8b
22         generic (n : integer := 8);

```

```

23
24     port ( R1,R2 : in signed ( n-1 downto 0 );
25           add_sub : in std_logic;
26           clk,Rst : in std_logic;
27           c_out : out std_logic;
28           ovf_det : out std_logic;
29           S : out signed ( n-1 downto 0 )
30     );
31 end component;
32
33 component hex_display
34   port( SW : in signed (3 downto 0);
35         HEXA : out std_logic_vector ( 0 to 6)
36   );
37 end component;
38
39 signal c_out : std_logic;
40
41
42 begin
43
44   ADD: reg_adder_8b port map(SW(15 downto 8), SW(7 downto 0), SW(16),
45                             KEY1, KEY0, c_out, LEDG8, LEDR);
46
47   --A display
48   HEXA7: hex_display port map(SW(15 downto 12),HEX7);
49   HEXA6: hex_display port map(SW(11 downto 8),HEX6);
50
51   --B display
52   HEXA5: hex_display port map(SW(7 downto 4),HEX5);
53   HEXA4: hex_display port map(SW(3 downto 0),HEX4);
54
55   --S display
56   HEXA1: hex_display port map(LEDR(7 downto 4),HEX1);
57   HEXA0: hex_display port map(LEDR(3 downto 0),HEX0);
58
59 end architecture;

```

Code 2.5: adder_display.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity adder_display_tb is
6 end adder_display_tb;
7
8

```

```

9  architecture struct of adder_display_tb is
10
11     component adder_display
12     port (
13         SW : in signed ( 16 downto 0 );
14         KEY1,KEY0 : in std_logic;
15         LEDG8 : out std_logic;
16         LEDR : buffer signed ( 7 downto 0 );
17         HEX7,HEX6,HEX5,HEX4,HEX1,HEX0 : out std_logic_vector(0 to 6)
18     );
19 end component;
20
21 signal A : signed ( 7 downto 0 );
22 signal B : signed ( 7 downto 0 );
23 signal A_int,B_int : integer;
24 signal A_B : signed (16 downto 0);
25 signal add_sub,ovf_det_dut,clk,Rst : std_logic;
26 signal S_dut : signed ( 7 downto 0 );
27 signal S_int_dut,S_ref : integer;
28 signal HEX7_dut,HEX6_dut,HEX5_dut,HEX4_dut,HEX1_dut,HEX0_dut :
    std_logic_vector(0 to 6);
29
30
31 begin
32
33     process
34     begin
35         for i in 1 to 10 loop
36             clk <= '0';
37             wait for 2 ns;
38             clk <= '1';
39             wait for 2 ns;
40         end loop;
41     end process;
42
43     add_sub <= '0', '1' after 16 ns;
44     Rst <= '1','0' after 27 ns;
45
46     A <= "10111010", "01110110" after 5 ns, "01111101" after 9 ns,
        "10101000" after 15 ns,
47     "11110111" after 21 ns, "01000111" after 25 ns;
48
49     B <= "00011010", "01100110" after 5 ns, "00011101" after 9 ns,
        "11111000" after 15 ns,
50     "11110001" after 21 ns, "11010101" after 25 ns;
51
52     A_int <= to_integer(A);
53     B_int <= to_integer(B);
54
55     A_B <= add_sub & A & B;

```

```

56
57   ADD: adder_display port map (A_B, clk, Rst, ovf_det_dut, S_dut,
58                               HEX7_dut, HEX6_dut, HEX5_dut, HEX4_dut, HEX1_dut, HEX0_dut);
59
60   S_int_dut <= to_integer(S_dut);
61
62   with add_sub select
63     S_ref <=
64       to_integer(A + B) when '0',
65       to_integer(A - B) when others;
66
67 end architecture;

```

Code 2.6: adder_display_tb.vhd

Capitolo 3

16-bit RCA, Carry-Bypass Adder and Carry-Select Adder

3.1 Spiegazione teorica

Per ogni sezione di questo esercizio si è sostituito l'8-bit Adder usato nell'esercizio 1 con un carry-bypass adder per la sezione 2 e con un carry-select adder per la sezione 3.

3.2 Procedimento

Per la sezione 1 è stato riutilizzato il codice del primo esercizio settando il generic $n = 16$. Per ciò che concerne, invece, le sezioni 2 e 3, sono stati usati i blocchi di setup e carry propagation mostrato in **figura 3.1** e in **Code 3.10 - 3.11**.


 


Figura 3.1: setup and carry-prop blocks


Nel caso del CSA, vengono usati due carry propagation che ricevono gli stessi ingressi e forniscono risultati diversi in virtù del c_{in} .

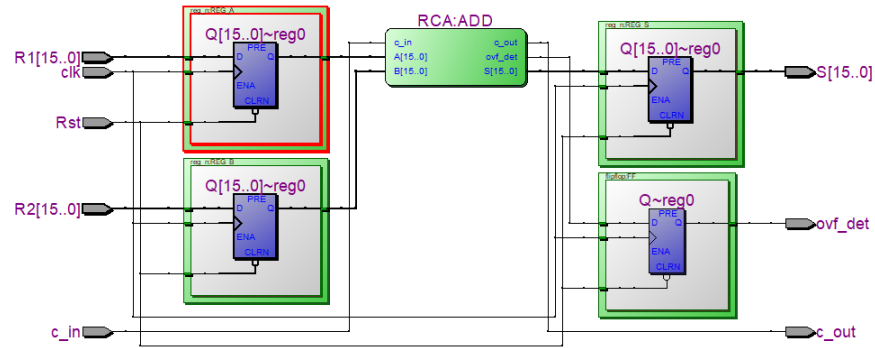3.3 Risultati


Di seguito sono mostrati i risultati prodotti da simulazione e sintesi.




(a) RTL viewer RCA 16 bit

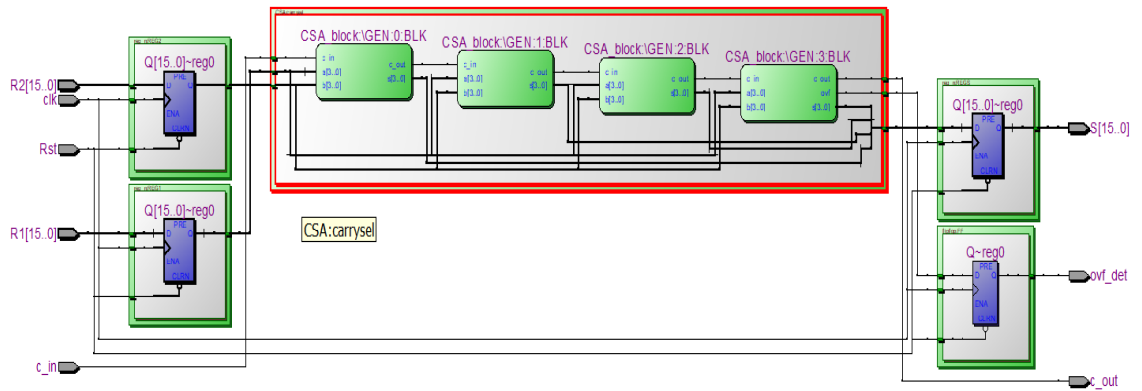


(b) RTL viewer CSA 16 bit

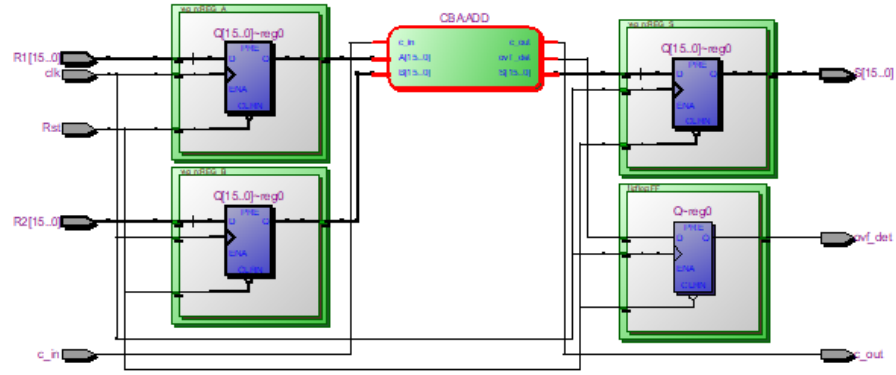


(c) RTL viewer BCA 16 bit

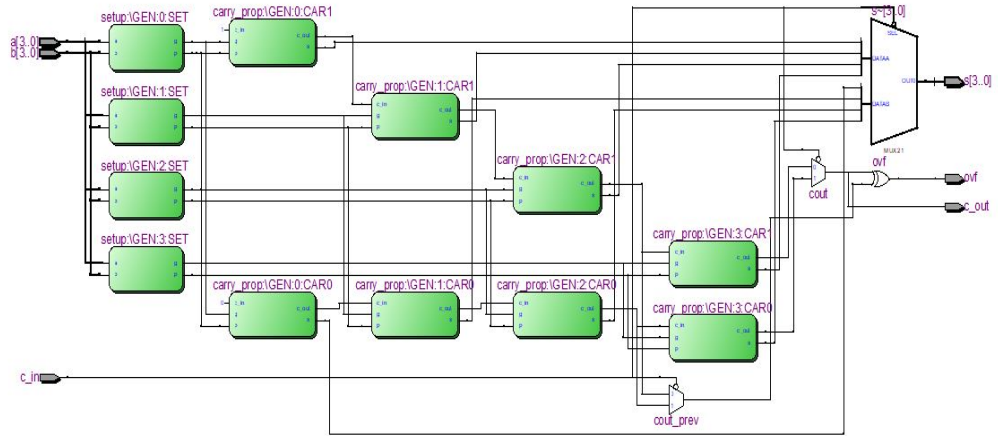

(d) RTL viewer CSA_block

 


(e) RTL viewer RCA adder

 


(f) RTL viewer CSA adder

Figure 3.2: RTL viewer exercise no. 3

 

(a) wave CBA

 


(b) wave CSA


Figure 3.3: waves exercise no. 3

Laddove si è riportata solo la sintesi dell'RCA a 16 bit poichè la simulazione ha lo stesso andamento di quella mostrata al capitolo 1, differendo solo del parallelismo.

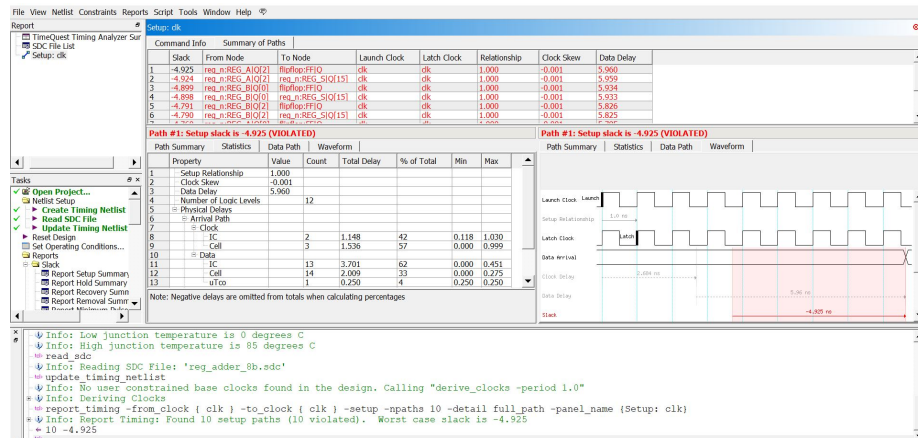
Di seguito, infine, i risultati della time analysis per i 3 sommatori in esame



(a) time analysis RCA 16 bit

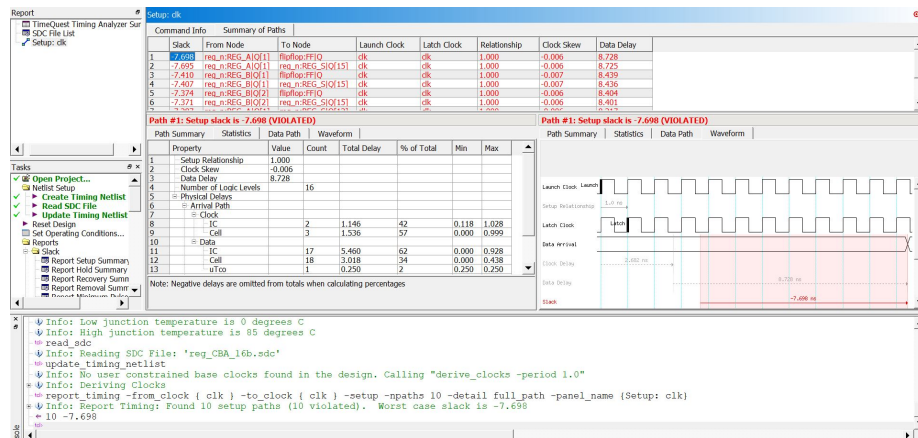

(b) time analysis CBA 16 bit

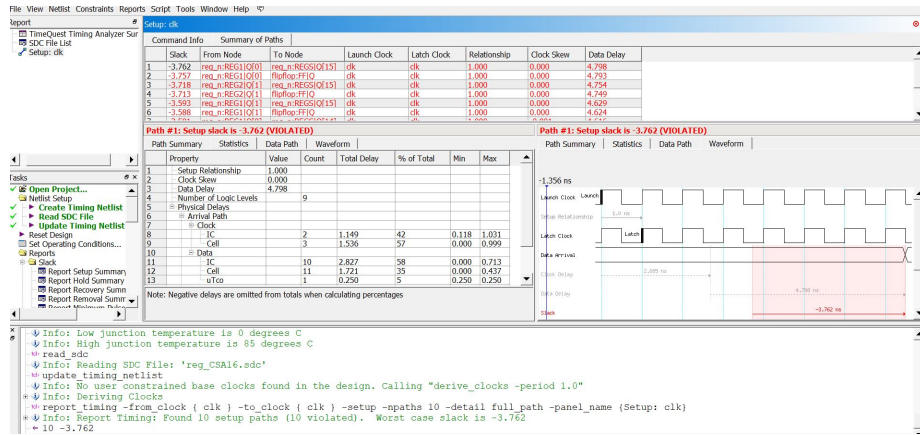

(c) time analysis CSA 16 bit

Figura 3.4: time analysis exercise no. 3

Laddove si evincono, rispettivamente

$$\begin{aligned}
 f_{max} &= 168.8 \text{ MHz} & t_{del} &= 5.96 \text{ ns} \\
 f_{max} &= 114.97 \text{ MHz} & t_{del} &= 8.73 \text{ ns} \\
 f_{max} &= 210 \text{ MHz} & t_{del} &= 4.80 \text{ ns}
 \end{aligned}$$

3.4 Appendice

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_CBA_16b is
6     port ( R1,R2 : in signed ( 15 downto 0 );
7           c_in : in std_logic;
8           clk,Rst : in std_logic;
9           c_out : out std_logic;
10          ovf_det : out std_logic;
11          S : out signed ( 15 downto 0 )
12        );
13 end reg_CBA_16b;
14
15 architecture struct of reg_CBA_16b is
16
17     component flipflop
18         port (D, Clock, Resetn : in std_logic;

```

```

19         Q : out std_logic
20     );
21 end component;
22
23
24 component reg_n
25     generic ( N : integer:=16);
26
27     port (R : in signed(N-1 downto 0);
28         Clock, Resetn : in std_logic;
29         Q : out signed(N-1 downto 0)
30     );
31 end component;
32
33
34
35 component CBA
36     port(
37         A,B : in signed( 15 downto 0 );
38         c_in : in std_logic;
39         S : out signed( 15 downto 0 );
40         c_out,ovf_det : out std_logic
41     );
42 end component;
43
44 signal A,B,Q : signed ( 15 downto 0 );
45 signal ovf : std_logic;
46
47 begin
48
49     REG_A: reg_n port map ( R1,clk,Rst,A);
50     REG_B: reg_n port map ( R2,clk,Rst,B);
51
52     ADD: CBA port map ( A,B,c_in,Q ,c_out,ovf);
53
54     FF: flipflop port map ( ovf,clk,Rst,ovf_det );
55
56     REG_S: reg_n port map (Q,clk,Rst,S);
57
58 end architecture;

```

Code 3.1: reg_CBA_16b.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_CBA_16b_tb is
6 end reg_CBA_16b_tb;

```

```

7
8
9
10 architecture struct of reg_CBA_16b_tb is
11
12     component reg_CBA_16b
13
14
15         port ( R1,R2 : in signed ( 15 downto 0 );
16               c_in : in std_logic;
17               clk,Rst : in std_logic;
18               c_out : out std_logic;
19               ovf_det : out std_logic;
20               S : out signed ( 15 downto 0 )
21             );
22
23     end component;
24
25     signal A,B : signed ( 15 downto 0 );
26     signal A_int,B_int : integer;
27     signal c_out_dut,ovf_det_dut,clk,Rst : std_logic;
28     signal S_dut : signed ( 15 downto 0 );
29     signal S_int_dut,S_ref : integer;
30
31
32 begin
33
34     process begin
35         for i in 1 to 10 loop
36             clk <= '0';
37             wait for 2 ns;
38             clk <= '1';
39             wait for 2 ns;
40         end loop;
41     end process;
42
43     Rst <= '1','0' after 27 ns;
44
45     A <= "1011101010111010", "0111011010111010" after 5 ns,
46         "1011101001111101" after 9 ns, "1010100010101000" after 15 ns,
47         "1111011101010001" after 21 ns, "0100101010000111" after 25 ns;
48
49     B <= "0001100110011010", "0110011001100110" after 5 ns,
50         "0001110100011101" after 9 ns, "1100011101111000" after 15 ns,
51         "1110001110110001" after 21 ns, "1000111011010101" after 25 ns;
52
53     A_int <= to_integer(A);
54     B_int <= to_integer(B);

```

```

55     ADD: reg_CBA_16b port map (A, B, '0', clk, Rst, c_out_dut,
        ovf_det_dut, S_dut);
56
57     S_int_dut <= to_integer(S_dut);
58     S_ref <= to_integer(A + B);
59
60 end architecture;

```

Code 3.2: reg_CBA_16b_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5
6  entity CBA is
7      port(
8          A,B : in signed( 15 downto 0 );
9          c_in : in std_logic;
10         S : out signed( 15 downto 0 );
11         c_out,ovf_det : out std_logic
12     );
13 end CBA;
14
15
16 architecture behaviour of CBA is
17
18     component setup
19         port( a,b : in std_logic;
20             p,g : out std_logic
21         );
22     end component;
23
24
25     component carry_prop
26         port( p,g,c_in : in std_logic;
27             s,c_out : out std_logic
28         );
29     end component;
30
31     signal P,G : std_logic_vector ( 15 downto 0 );
32     signal carries : std_logic_vector ( 20 downto 0 );
33     signal sel : std_logic_vector ( 3 downto 0 );
34
35
36 begin
37
38     carries(0) <= c_in;
39

```

```

40  GEN: for i in 0 to 3 generate
41
42      -- whole CBA ovf check
43      HDHDH: for j in 0 to 3 generate
44
45          SET: setup port map ( A(4*i+j),B(4*i+j),P(4*i+j),G(4*i+j) );
46
47          CA_PROP: carry_prop port map ( P(4*i+j),G(4*i+j),carries(5*i+j),S(4*i
              +j),carries(5*i+j+1) );
48
49          end generate;
50
51      -- check on propagate value
52      sel(i) <= P(4*i) and P(4*i+1) and P(4*i+2) and P(4*i+3);
53      carries(i*5 + 5) <= carries(i*5+4) when (sel(i) = '0') else
          carries(i*5);
54
55      end generate;
56
57      c_out <= carries(20);
58      ovf_det <= carries(18) xor carries(19);
59
60  end architecture;

```

Code 3.3: CBA.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity CBA_tb is
6  end CBA_tb;
7
8
9
10 architecture struct of CBA_tb is
11
12     component CBA
13     port(
14         A,B : in signed( 15 downto 0 );
15         c_in : in std_logic;
16         S : out signed( 15 downto 0 );
17         c_out,ovf_det : out std_logic
18         );
19     end component;
20
21     signal A : signed ( 15 downto 0 );
22     signal B : signed ( 15 downto 0 );
23     signal A_int,B_int : integer;

```

```

24  signal c_out_dut,ovf_det_dut : std_logic;
25  signal S_dut : signed ( 15 downto 0 );
26  signal S_ref,S_int_dut : integer;
27
28  begin
29  process begin
30      for i in 2 to 4 loop
31
32          A <= to_signed(63*i, A'length);
33
34          for j in 0 to 2 loop
35
36              B <= to_signed(61*j, B'length);
37              wait for 2 ns;
38
39          end loop;
40
41      end loop;
42
43  end process;
44
45  A_int <= to_integer(A);
46  B_int <= to_integer(B);
47  BCA: CBA port map (A,B,'0',S_dut,c_out_dut,ovf_det_dut);
48
49  S_int_dut <= to_integer(S_dut);
50  S_ref <= to_integer(A + B) ;
51
52  end architecture;

```

Code 3.4: CBA_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity reg_CSA16 is
6      generic (n : integer := 16);
7      port (
8          R1,R2 : in signed ( n-1 downto 0 );
9          c_in : in std_logic;
10         clk,Rst : in std_logic;
11         c_out : out std_logic;
12         ovf_det : out std_logic;
13         S : out signed ( n-1 downto 0 )
14     );
15  end reg_CSA16;
16
17

```



```

18 architecture behavior of reg_CSA16 is
19
20     component flipflop
21     port (
22         D, Clock, Resetn : in std_logic;
23         Q : out std_logic
24     );
25 end component;
26
27 component reg_n
28     generic ( N : integer:=n);
29     port (
30         R : in signed(N-1 downto 0);
31         Clock, Resetn : in std_logic;
32         Q : out signed(N-1 downto 0)
33     );
34 end component;
35
36 component CSA
37     port(
38         A,B : in signed( 15 downto 0 );
39         c_in : in std_logic;
40         S : out signed( 15 downto 0 );
41         c_out,ovf_det : out std_logic
42     );
43 end component;
44
45 signal a,b,q : signed(n-1 downto 0);
46 signal ovfl : std_logic;
47
48 begin
49
50     REG1: reg_n port map (R1, clk, rst, a);
51     REG2: reg_n port map (R2, clk, rst, b);
52     carrysel: CSA port map (a, b, c_in, q, c_out, ovfl);
53     FF: flipflop port map (ovfl, clk, rst, ovf_det);
54     REGS: reg_n port map(q, clk, rst, S);
55
56 end behavior;

```

Code 3.5: reg_CSA16.vhd

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity reg_csa16_tb is
6 end reg_csa16_tb;
7

```

```

8  architecture test of reg_csa16_tb is
9
10  component reg_CSA16 is
11  generic (n : integer := 16);
12  port (
13      R1,R2 : in signed ( n-1 downto 0 );
14      c_in : in std_logic;
15      clk,Rst : in std_logic;
16      c_out : out std_logic;
17      ovf_det : out std_logic;
18      S : out signed ( n-1 downto 0 )
19  );
20  end component;
21
22  signal A,B : signed ( 15 downto 0 );
23  signal A_int,B_int : integer;
24  signal cin, c_out_dut,ovf_det_dut,clk,Rst : std_logic;
25  signal S_dut : signed ( 15 downto 0 );
26  signal s_int_dut, S_ref : integer;
27
28
29  begin
30
31  process begin
32      for i in 1 to 10 loop
33          clk <= '0';
34          wait for 2 ns;
35          clk <= '1';
36          wait for 2 ns;
37      end loop;
38  end process;
39
40  rst <= '1', '0' after 5 ns, '1' after 10 ns;
41
42  --input values
43  A <= "0000000000000001", "1000000000000001" after 3 ns,
44      "1000000000001111" after 11 ns,
45      "0101010101010101" after 15 ns, "0101010101010101" after 21 ns,
46      "0100101010000111" after 25 ns;
47
48  B <= "0000000000000101", "1000000000000000" after 3 ns,
49      "1000000000000000" after 11 ns,
50      "1010101000101010" after 15 ns, "0000000000000011" after 21 ns,
51      "1000111011010101" after 25 ns;
52
53  cin <= '0', '1' after 5 ns, '1' after 10 ns, '0' after 15 ns, '1'
54      after 20 ns;
55
56  DUT: reg_CSA16 port map (A, B, cin, clk, rst, c_out_dut, ovf_det_dut,
57      s_dut);

```

```

52
53     A_int <= to_integer(A);
54     B_int <= to_integer(B);
55
56     S_int_dut <= to_integer(S_dut);
57     S_ref <= to_integer(A + B);
58
59 end test;

```

Code 3.6: reg_CSA16_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5
6  entity CSA is
7      port(
8          A,B : in signed( 15 downto 0 );
9          c_in : in std_logic;
10         S : out signed( 15 downto 0 );
11         c_out,ovf_det : out std_logic
12     );
13 end CSA;
14
15
16
17 architecture behaviour of CSA is
18
19     component CSA_block
20     port(
21         a,b : in signed( 3 downto 0 );
22         c_in : in std_logic;
23         s : out signed( 3 downto 0 );
24         c_out, ovf : out std_logic
25     );
26 end component;
27
28     signal carries : std_logic_vector ( 4 downto 0 );
29     signal ovfs : std_logic_vector(3 downto 0);
30
31 begin
32
33     carries(0) <= c_in;
34
35     GEN: for i in 0 to 3 generate
36
37         BLK: CSA_block port map (A((i*4+3) downto i*4), B( (i*4+3) downto
            i*4), carries(i),

```

```

38             s((i*4+3) downto i*4),carries(i+1), ovfs(i));
39
40     end generate;
41
42     c_out <= carries(4);
43     ovf_det <= ovfs(3);
44
45 end architecture;

```

Code 3.7: CSA.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity csa_tb is
6  end csa_tb;
7
8  architecture test of csa_tb is
9
10     component CSA
11     port(
12         A,B : in signed( 15 downto 0 );
13         c_in : in std_logic;
14         S : out signed( 15 downto 0 );
15         c_out,ovf_det : out std_logic
16     );
17 end component;
18
19 signal in1, in2, sum, sum_ref : signed(15 downto 0);
20 signal cin, cout, cout_ref, ovf, ovf_ref : std_logic;
21
22 begin
23     --input values
24     in1 <= "0000000000000001", "1000000000000001" after 5 ns,
25           "0000000000001111" after 10 ns,
26           "01010101010101" after 15 ns, "01010101010101" after 20 ns;
27
28     in2 <= "0000000000000101", "1000000000000000" after 5 ns,
29           "1000000000000000" after 10 ns,
30           "1010101000101010" after 15 ns, "0000000000000011" after 20 ns;
31
32     cin <= '0', '1' after 5 ns, '1' after 10 ns, '0' after 15 ns, '1'
33           after 20 ns;
34
35     --expected outputs
36     sum_ref <= "000000000000110", "000000000000010" after 5 ns,
37              "1000000000010000" after 10 ns,
38              "111111101111111" after 15 ns, "01010101011001" after 20 ns;

```

```

35
36     cout_ref <= '0', '1' after 5 ns, '0' after 10 ns, '0' after 15 ns,
        '0' after 20 ns;
37
38     ovf_ref <= '0', '1' after 5 ns, '0' after 10 ns, '0' after 15 ns,
        '0' after 20 ns;
39
40     DUT: CSA port map (in1, in2, cin, sum, cout, ovf);
41
42 end test;

```

Code 3.8: CSA_tb.vhd

```

1
2 library ieee;
3 use ieee.std_logic_1164.all;
4 use ieee.numeric_std.all;
5
6
7 entity CSA_block is
8     port(
9         a,b : in signed( 3 downto 0 );
10        c_in : in std_logic;
11        s : out signed( 3 downto 0 );
12        c_out, ovf : out std_logic
13    );
14 end CSA_block;
15
16 architecture behaviour of CSA_block is
17
18     component setup
19         port( a,b : in std_logic;
20             p,g : out std_logic
21         );
22     end component;
23
24
25     component carry_prop
26         port( p,g, c_in : in std_logic;
27             s,c_out : out std_logic
28         );
29     end component;
30
31
32     signal p,g : std_logic_vector ( 3 downto 0 );
33     signal carries_0,carries_1 : std_logic_vector ( 4 downto 0 );
34     signal sum_0,sum_1 : signed ( 3 downto 0 );
35     signal cout, cout_prev : std_logic;
36

```

```

37 begin
38
39     carries_0(0) <= '0';
40     carries_1(0) <= '1';
41
42     GEN: for i in 0 to 3 generate
43
44         SET: setup port map ( a(i), b(i), p(i), g(i) );
45         CAR0: carry_prop port map ( p(i), g(i), carries_0(i), sum_0(i),
46                                     carries_0(i+1));
47         CAR1: carry_prop port map ( p(i), g(i), carries_1(i), sum_1(i),
48                                     carries_1(i+1));
49
50     end generate;
51
52     cout <= carries_0(4) when (c_in = '0') else carries_1(4);
53     cout_prev <= carries_0(3) when (c_in = '0') else carries_1(3);
54
55     c_out <= cout;
56     ovf <= cout xor cout_prev;
57
58     s <= sum_0 when (c_in = '0') else sum_1;
59
60 end architecture;

```

Code 3.9: CSA_block.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity carry_prop is
6      port( p,g,c_in : in std_logic;
7            s,c_out  : out std_logic
8            );
9  end carry_prop;
10
11 architecture logic of carry_prop is
12
13 begin
14
15     s <= c_in xor p;
16     c_out <= g or ( p and c_in );
17
18 end architecture;

```

Code 3.10: carry_prop.vhd

1

```

2  library ieee;
3  use ieee.std_logic_1164.all;
4  use ieee.numeric_std.all;
5
6  entity setup is
7      port( a,b : in std_logic;
8            p,g : out std_logic
9            );
10 end setup;
11
12 architecture logic of setup is
13
14 begin
15
16     g <= a and b;
17     p <= a xor b;
18
19 end architecture;

```

Code 3.11: setup.vhd

Capitolo 4

Multiplier

4.1 Spiegazione teorica

In quest'ultimo capitolo, ci proponiamo di implementare un moltiplicatore di ingressi unsigned di parallelismo 4, per la realizzazione del quale ci si è serviti dell' RCA implementato nel secondo esercizio, modificando opportunamente i tipi (da signed ad unsigned).

4.2 Procedimento

Lo schema a blocchi a partire dal quale si è implementato il circuito è mostrato in **figura 4.1**, nel quale si evidenzia la struttura globale del circuito. Rispetto alla notazione utilizzata in **Code 4.1**, per questioni grafiche, i segnali intermedi sono stati chiamati genericamente "A(i)" e "B(i)".

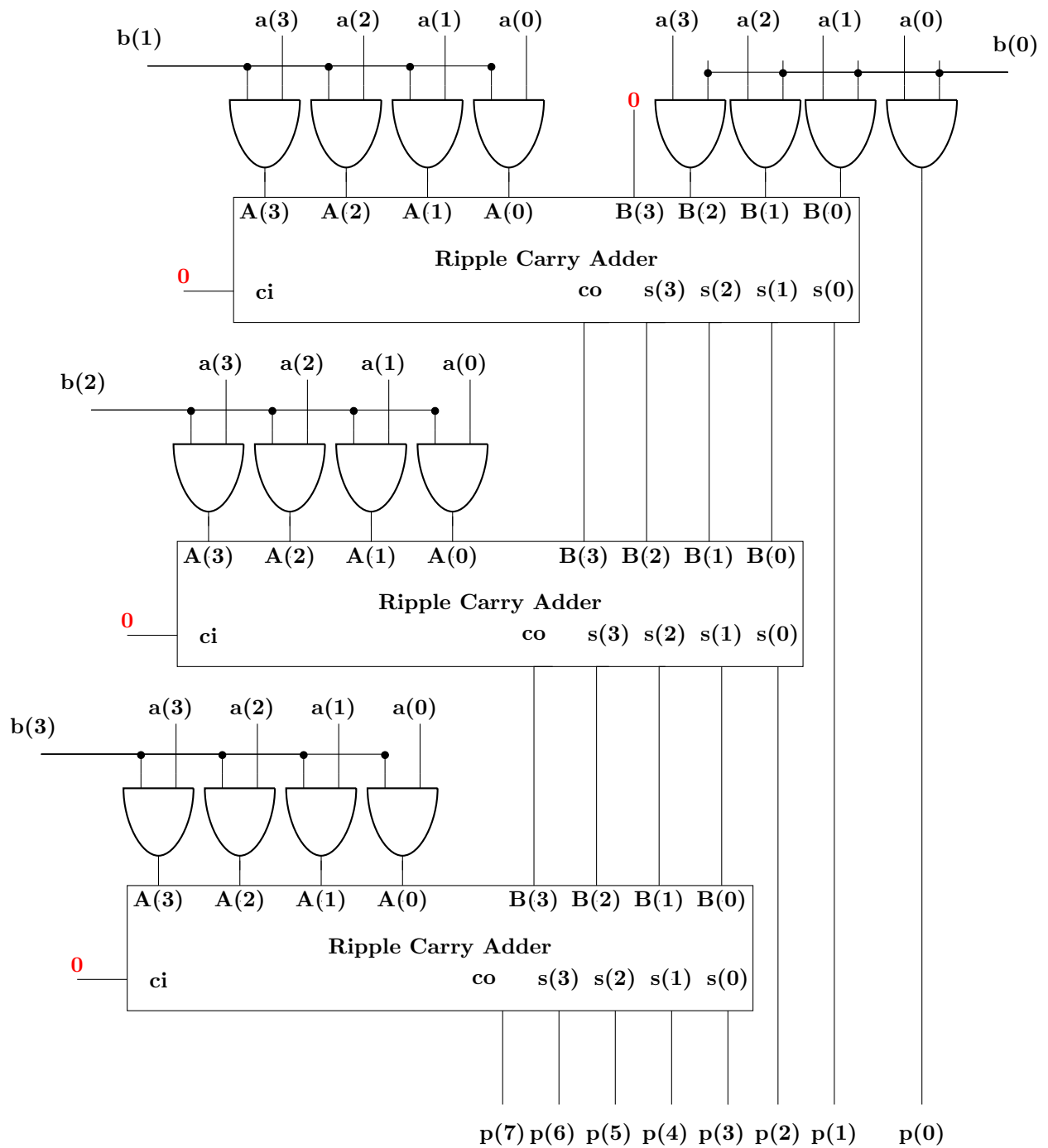


Figura 4.1: 4bit-Multiplier block scheme

4.3 Risultati

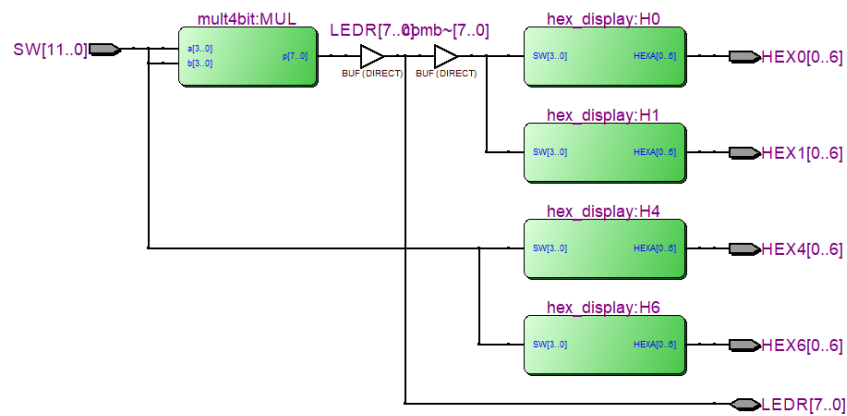


Figura 4.2: RTL viewer exercise no. 4

 


Figura 4.3: wave exercise no. 4

4.4 Appendice

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity mult4bit is
6     port(
```

```

7      a, b : in unsigned(3 downto 0);
8      p : out unsigned (7 downto 0)
9  );
10 end mult4bit;
11
12
13 architecture behaviour of mult4bit is
14     component RCA
15     port(
16         a,b : in unsigned(3 downto 0);
17         s : out unsigned(3 downto 0);
18         cout : out std_logic
19     );
20 end component;
21
22 signal AND0, AND1, AND2 : unsigned (3 downto 0); -- ANDs input to RCAs
23 signal B0, B1, B2 : unsigned (3 downto 0); -- intermediate signals
24     between RCAs
25 begin
26
27     B0 <= ('0', a(3) and b(0), a(2) and b(0), a(1) and b(0));
28
29     -- bitwise AND generating correct dimension range
30     -- for R values of AND operand
31     AND0 <= a and (AND0'range => b(1));
32     AND1 <= a and (AND1'range => b(2));
33     AND2 <= a and (AND2'range => b(3));
34
35
36     -- evaluating outputs
37     p(0) <= a(0) and b(0);
38     RCA0: RCA port map (
39         a => AND0,
40         b => B0,
41         cout => B1(3),
42         s(3 downto 1) => B1(2 downto 0),
43         s(0) => p(1)
44     );
45
46     RCA1: RCA port map (
47         a => AND1,
48         b => B1,
49         cout => B2(3),
50         s(3 downto 1) => B2(2 downto 0),
51         s(0) => p(2)
52     );
53
54     RCA2: RCA port map (
55         a => AND2,

```

```

56         b => B2,
57         cout => p(7), -- last bit = carry out
58         s => p(6 downto 3)
59     );
60
61 end architecture;

```

Code 4.1: mult4bit.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity mult4bit_tb is
6  end mult4bit_tb;
7
8
9  architecture testcase of mult4bit_tb is
10     component mult4bit is
11     port(
12         a, b : in unsigned(3 downto 0);
13         p : out unsigned (7 downto 0)
14     );
15     end component;
16
17     signal a_dut, b_dut : unsigned(3 downto 0);
18     signal p_dut, p_ref : unsigned(7 downto 0);
19
20
21
22     begin
23         UUT : mult4bit port map (a_dut, b_dut, p_dut);
24
25         -- test cases (all combinations of two 4 bit wide inputs)
26         process begin
27             for i in 0 to 15 loop
28
29                 a_dut <= to_unsigned(i, a_dut'length);
30
31                 for j in 0 to 15 loop
32                     b_dut <= to_unsigned(j, b_dut'length);
33                     wait for 0 ns;
34                     p_ref <= a_dut * b_dut; -- works bc they're both unsigned !!
35                     wait for 5 ns;
36                 end loop;
37             end loop;
38         end process;
39
40     end process;

```

```

41
42 end architecture;

```

Code 4.2: mult4bit_tb.vhd

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity mult4bit_synth is
6      port(
7          SW : in unsigned (11 downto 0);
8          LEDR : buffer unsigned (7 downto 0);
9          HEX6 : out std_logic_vector(0 to 6);
10         HEX4 : out std_logic_vector(0 to 6);
11         HEX1 : out std_logic_vector(0 to 6);
12         HEX0 : out std_logic_vector(0 to 6)
13     );
14 end mult4bit_synth;
15
16 architecture behaviour of mult4bit_synth is
17
18     component mult4bit is
19         port(
20             a, b : in unsigned(3 downto 0);
21             p : out unsigned (7 downto 0)
22         );
23     end component;
24
25     component hex_display is
26         port(
27             SW : in unsigned (3 downto 0);
28             HEXA : out std_logic_vector ( 0 to 6)
29         );
30     end component;
31
32     begin
33         MUL : mult4bit port map(SW(11 downto 8), SW(3 downto 0), LEDR);
34
35         H6 : hex_display port map(SW(11 downto 8), HEX6);
36         H4 : hex_display port map(SW(3 downto 0), HEX4);
37         H1 : hex_display port map(LEDR (7 downto 4), HEX1); -- last 4 bits
38             on HEX1
39         H0 : hex_display port map(LEDR(3 downto 0), HEX0); -- first 4 bits
39             on HEX0
40     end architecture;

```

Code 4.3: mult4b_synth.vhd
